
Lab 1

Name: BUGGITINA.SHIVA KUMAR

Enrollment No: 92301733056

CO1: Develop fundamentals in fabrication of MOSFETs and MOS transistor

CO2: Analyze MOS inverters with its static and switching characteristics

CO3: Analyze Combinational and Sequential MOS logic circuit


Experiment 1: Introduction to LTSPICE Tool & Microwind Tool

Basic Circuit Simulation with LTspice

A flexible, precise, and cost-free circuit simulator for Windows and Mac is called LTSpice. It introduces AC and DC simulation and details the analysis of digital circuits' output signals.

Getting Started

 
Visit the Linear Technology design tools website (www.analog.com) to download a copy of the LTSpice executable. When the software is installed and running, you will see a screen similar to the one below. You must first make a new draught by clicking the tiny red "LT" icon next to the file option in order to start creating a schematic:



You may begin adding and altering components from here, but let's first go through some keyboard shortcuts. The majority of these are located on the toolbar above the circuit window or, if you prefer, in the "Edit" and "View" menus. There is a significant collection of resources, including further usage examples, in the Help menu if you ever run into trouble using LTSpice. Some hotkeys for building your schematic are listed below:

R: Place Resistor	F2: Component Menu	F7: Move without Wires
C: Place Capacitor	F3: Draw Wire	F8: Drag/Move with wires
L: Place Inductor	F4: Label Net	F9: Undo (Shift + F9)
D: Place Diode	F5: Delete	CTRL+R: Rotate
G: Place Ground	F6: Copy	CTRL+E: Mirror

CTRL+Z and CTRL+B are used to zoom in and out, respectively; CTRL+Z does not undo. By pressing the spacebar, you may "zoom to fit," which elegantly adjusts the viewing area. Launch a new schematic editor and begin the circuit simulation using LTSpice. Click the new schematic under File. A CMOS inverter must have the following components: NMOS, PMOS, a voltage source, wire, capacitor, and ground. Place the NMOS and PMOS in the schematic now. When you click on the component symbol, a list of component symbols will appear for you to choose from. Choose NMOS and PMOS.

 

On the schematic, put it anywhere. The following step is to access the component menu once more and select a different voltage source from the component menu's top level (you can save time by using the copy hotkey after placing the first).

DC Characteristics of CMOS Inverter



With the help of the LTSpice circuit modeling tool, we will simulate the CMOS inverter. In order to simulate the CMOS inverter circuit, we will use the BSIM4 Spice model.

What is BSIM4?

BSIM, also known as the Berkeley short-channel IGFET model, first gained popularity in 1987. The following steps are involved in modeling any device.

- Processing or fabrication technique.
- Device simulation emphasizes device physics.
- Characterization of the device.
- Transform into software programming.

The first industrially accepted MOSFET model, BSIM, is also the first CMC standard model in TM12, allowing for effective macro modeling. The BSIM model's success can be attributed to Professor Don Peterson giving the industry free use of the Spice model. 90% of integrated circuits are made using CMOS technology, and CMOS inverters are the fundamental component of every digital circuit. Use the 4 terminal NMOS and PMOS device, which uses the symbol to indicate the substrate is p-type to n channel, to place the PMOS and NMOS on the schematic with the MOSFET terminal source connected to the bulk. Set the PMOS and NMOS sizes by selecting the MOSFET from the context menu, as seen in the image below. According to the BSIM model file used in our experiment, give the model the names P1 and N1.

  

The logical operation of CMOS inverter

Input	Output
Low	High
High	Low

```
models.txt - Notepad
File Edit Format View Help
*
* Short channel models from CMOS Circuit Design, Layout, and Simulation,
* 50nm BSIM4 models VDD=1V, see CMOSedu.com
*
.model N_50n nmos level = 54
+binunit = 1 paramchk = 1 mobmod = 0
+capmod = 2 igcmod = 1 igbmod = 1 geomod = 0
+diomod = 1 rdsmod = 0 rbodymod = 1 rgatemod = 1
+permod = 1 acnqsmod = 0 trnqsmod = 0
+tnom = 27 tox = 1.4e-009 toxp = 7e-010 toxm = 1.4e-009
+epsrox = 3.9 wint = 5e-009 lint = 1.2e-008
+ll = 0 wl = 0 llm = 1 wln = 1
+lw = 0 ww = 0 lwn = 1 wwn = 1
+lw1 = 0 ww1 = 0 xpart = 0 toxref = 1.4e-009
+vth0 = 0.22 k1 = 0.35 k2 = 0.05 k3 = 0
+k3b = 0 w0 = 2.5e-006 dvt0 = 2.8 dvt1 = 0.52
+dvt2 = -0.032 dvt0w = 0 dvt1w = 0 dvt2w = 0
+dsb = 2 minv = 0.05 voff1 = 0 dvtp0 = 1e-007
+dvtp1 = 0.05 lpe0 = 5.75e-008 lpeb = 2.3e-010 xj = 2e-008
+ngate = 5e+020 ndep = 2.8e+018 nsd = 1e+020 phin = 0
+cdsc = 0.0002 cdscb = 0 cdsd = 0 cit = 0
+voff = -0.15 nfactor = 1.2 eta0 = 0.15 etab = 0
+vfb = -0.55 u0 = 0.032 ua = 1.6e-010 ub = 1.1e-017
+uc = -3e-011 vsat = 1.1e+005 a0 = 2 ags = 1e-020
+a1 = 0 a2 = 1 b0 = -1e-020 bl = 0
+keta = 0.04 dwg = 0 dwb = 0 pclm = 0.18
+pdiblc1 = 0.028 pdiblc2 = 0.022 pdiblc3 = -0.005 drout = 0.45
+pvag = 1e-020 delta = 0.01 pscbe1 = 8.14e+008 pscbe2 = 1e-007
+fprout = 0.2 pdits = 0.2 pditsd = 0.23 pdits1 = 2.3e+006
+rsh = 3 rds = 150 rsw = 150 rdw = 150
+rdswmin = 0 rdswmin = 0 rswmin = 0 prwg = 0
+prwb = 6.8e-011 wr = 1 alpha0 = 0.074 alpha1 = 0.005
+beta0 = 30 agidl = 0.0002 bgidl = 2.1e+009 cgidl = 0.0002
+egidl = 0.8
+aigbacc = 0.012 bigbacc = 0.0028 cigbacc = 0.002
+nigbacc = 1 aigbinv = 0.014 bigbinv = 0.004
+eigbinv = 1.1 nigbinv = 3 aigc = 0.017 bigc = 0.0028
+cigc = 0.002 aigsd = 0.017 bigsd = 0.0028 cigsd = 0.002
```

Monolithic MOSFET - M2

Model Name: P1 OK Cancel

Length(L): 100n

Width(W): 500n

Drain Area(AD):

Source Area(AS):

Drain Perimeter(PD):

Source Perimeter(PS):

No. Parallel Devices(M):

P1 L=100n w=500n

Monolithic MOSFET - M1

Model Name: N1 OK Cancel

Length(L): 50n

Width(W): 500n

Drain Area(AD):

Source Area(AS):


Drain Perimeter(PD):

Source Perimeter(PS):

No. Parallel Devices(M):



N1 L=50n w=500n

 
To include the BSIM model file, Go to edit and select SPICE Directive's' and then type .include model.txt.




The VDD and digital ground must be defined as input pins in this work, as illustrated in the fig below. Give an input or output port type definition.

  Label the output as OUT and the input as IN. When the CMOS inverter input is linked to ground, the output is pushed through the ground by the NMOS device and is pulled to VDD by the PMOS device when the input is connected to VDD.




 

 The first source of sweep will be V2, the start value to be 0, and stop value as 5 with 0.01 increment.



 Let us place the SPICE analysis on the schematic and run the simulation. Region 1 of the DC characteristics, the input voltage is low, the NMOS is OFF, and PMOS is ON. As the input voltage increases, both the NMOS and PMOS turn ON. When the input voltage increased further, PMOS turns OFF, and NMOS fully turns ON.





Microwind Tool:


The MICROWIND2 program allows the student to design and simulate an integrated circuit at physical description level. The package contains a library of common logic and analog ICs to view and simulate. MICROWIND2 includes all the commands for a mask editor as well as original tools never gathered before in a single module (2D and 3D process view, VERILOG compiler, tutorial on MOS devices). You can gain access to Circuit Simulation by pressing one single key. The electric extraction of your circuit is automatically performed and the analog simulator produces voltage and current curves immediately.

Open the layout editor window in Microwind. Click File -> Select Foundry and select X.rul. This sets your layout designs in X technology.

  Click on Compile -> Compile Verilog File. An Open Window appears. Select the .txt verilog file saved before and open it.




 After selecting the .txt file, a new window appears called Verilog file. Click on Size on the right top menus. This shows up the NMOS and PMOS sizes. Set the sizes according to choose.




Click Compile and then Back to editor in the Verilog File Window. This creates a layout in layout editor window using automatic layout generation procedure.

 Add a capacitance to the output of the design. The value of the capacitance depends on your choice.




Click on OK. The capacitance is shown on the left bottom corner with a value of 0.015fF.

 Click on the label marked In1. A window appears. Click on the Pulse option in the window. Insert a 01 sequence for that specific input and click on Insert. Then click on Assign. Perform this assignment on the other inputs.





 Click Simulate -> Run simulation. A simulation window appears with inputs and output, shows the t_{phl} , t_{plh} and t_p of the circuit. The power consumption is also shown on the right bottom portion of the window. • If you are unable to meet the specifications of the circuit change the transistor sizes. Generate the layout again and run the simulations till you achieve your target delays.





Design the layout manually

  Open the layout editor window in Microwind. Click File -> Select Foundry and select X.rul
Vdd and GND rails are of Metal1. The top rail is used as Vdd and the bottom one as GND.
Click on Metal 1 in the palette and then create the required rectangle in the layout window





  The next step is to build the NMOS transistors. Click on the transistor symbol in the palette. Set the W, L of the transistor. Then click on Generate device. The source of the transistor is connected to the GND rail





Create another NMOS and place it in parallel to the first NMOS device. We share the two devices' drain diffusions. A DRC check can be run by clicking on Analysis -> Design Rule Checker.

  The next step is to place two PMOS transistors in series





Place the PMOs transistor on layout close to the Vdd rail on the top. To construct two PMOS transistors in series, diffusions are shifted to a side and another poly line is added as second transistor. The diffusion is shared to save area and reduce capacitance.

 
 
The next step is to connect the inputs and the output of the two transistors.



  
Poly inputs are connected. Metal output is connected. The next step is to connect the poly to metal1 and then to metal2. The first symbol in the first row of the palette is the poly to metal1 contact.



 
 
Then we connect the metal1 to metal2 contact to the previous contact. This is the 4th contact on the first row. The next step is to connect the output Metal1 to Metal2. Once again use the 4th contact in the first row.




 
Now we connect metal2 to the two inputs and one output and bring them to the top to go out of the cell. Observe the two inputs (left & right) and an output (middle) above the Vdd rail in dark blue color.



  Now we label the inputs and output as In1, In2 and out. Click on Add a Pulse Symbol in the palette (5th from the right in the 3rd row). Then click on the metal2 of one of the inputs. A window appears. Change the name of the input signal. Insert 01 sequences and click on Insert. The click on Assign. Similarly assign the 2nd input a pulse.





  
Now select the Visible Node symbol from the palette (7th in the third row). Select it and click on the output. The 'Add a Visible Property' window appears. Change the label name to out. Select Visible in Simulation. Click on Assign. Now the output is also labeled.



Select Vdd Supply and GND from the palette (third row). Also click on the capacitor (3rd in 2nd row) symbol and add it to the output. Also, extend the pwell into the Vdd Rail. The click on Edit -> Generate -> Contacts. Select PATH and then in Metal choose Metal1 and N+ polarization.

  To run the Simulation of your circuit, click on Simulate -> Start Simulation. Depending on the input sequences assigned at the input the output is observed in the simulation. The power value is also given



 

Conclusion:

In this lab, we successfully explored two essential tools for VLSI design—LTSpice and Microwind. Using LTSpice, we simulated the DC characteristics of a CMOS inverter and gained practical insights into the working of NMOS and PMOS transistors. We learned how to construct and analyze the inverter circuit, observing the voltage transfer characteristics and understanding the logic levels of digital outputs.